


## Theorem 1: Norton's Theorem

### Statement :

Norton's Theorem states that a linear two terminal network can be replaced by an equivalent circuit consisting of a current  $I_N$  in parallel with a resistor  $R_N$ , where

- $R_N$  is the equivalent resistance at the terminals when the independent sources are turned off
- $I_N$  is short circuit current through the terminals.

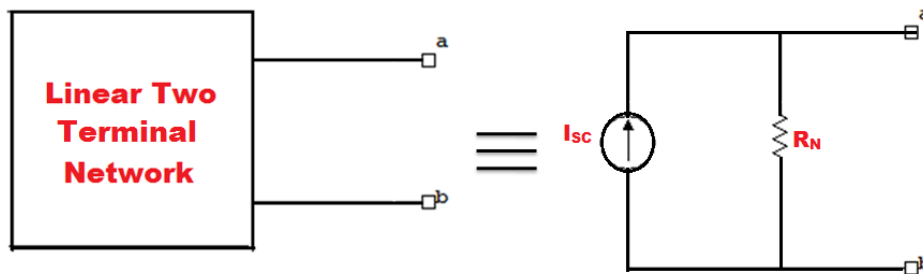If the circuit consists of the dependent sources the Norton's resistance has to be found out as  $R_N = V_{oc} / I_{sc}$




There can be two types of problems,

1. To find the Norton's equivalent circuit across the open circuit terminals
2. To find a voltage or a current in the circuit by Norton's Theorem.
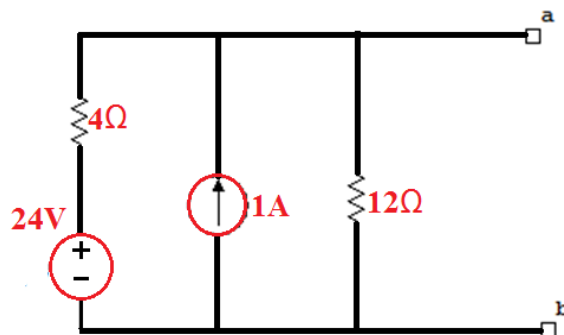
### Problems:

P1. Find the Norton's equivalent circuit across the terminals a-b




Solution:

Steps to find out the Norton's Resistance  $R_N$  :

Step 1: Turn off the independent sources

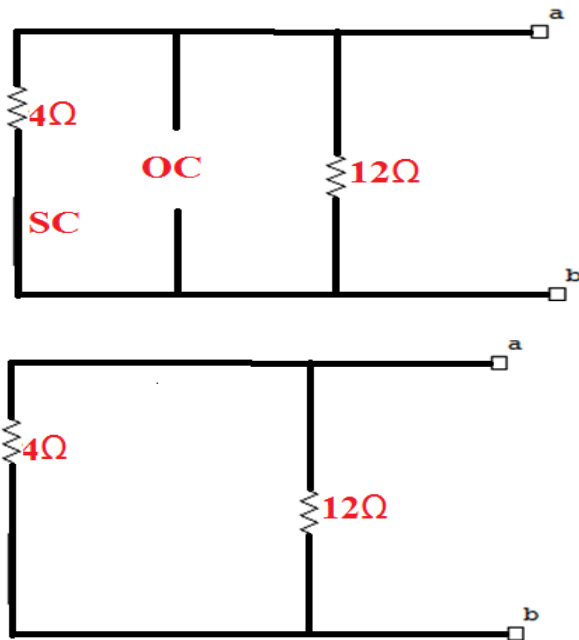(open-circuit the current source and short-circuit the voltage source)



Step 2: Find the equivalent resistance looking into the open circuit terminals


$$R_N = 12 \times 4 / 12 + 4$$

$$R_N = 3 \Omega$$


Steps to find out the Norton's Current  $I_N$  (Short circuit current):

Step 1: Short circuit the open circuit terminals and mark the  $I_{SC}$  as shown.

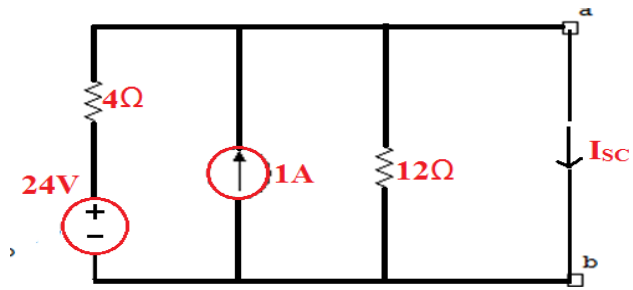Step 2: Find the short circuit current by a suitable technique



By Node Analysis:

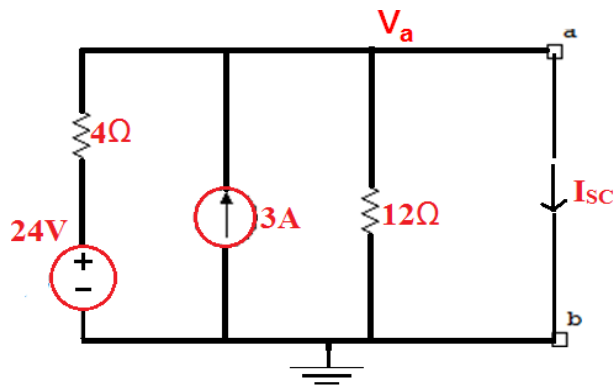


Applying KCL at node a :

$$\frac{V_a - 24}{4} + \frac{V_a}{12} + I_{sc} = 3$$


Substituting  $V_a = 0$  V in the above equation implies

$$I_{sc} = 9 \text{ A}$$

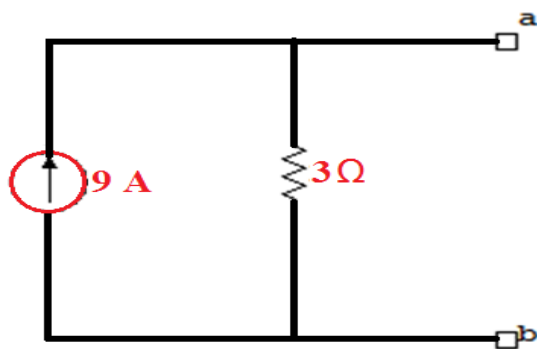Therefore the Norton's equivalent circuit across terminals a-b is



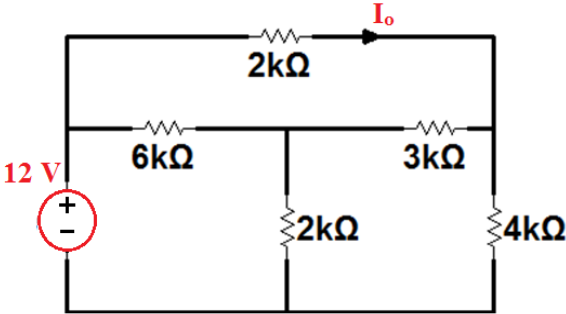P2. Find  $I_0$  in the network shown, using Norton's Theorem






Solution:

Step 1: Separate the branch through which  $I_0$  is flowing


Step 2: Find the Norton's equivalent network across the open circuit terminals

Step 3: Connect the branch separated, back to the Norton's equivalent circuit to find  $I_0$

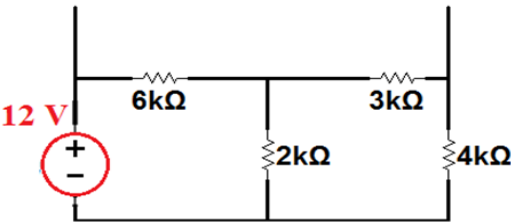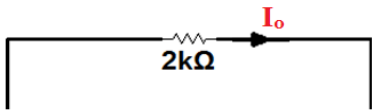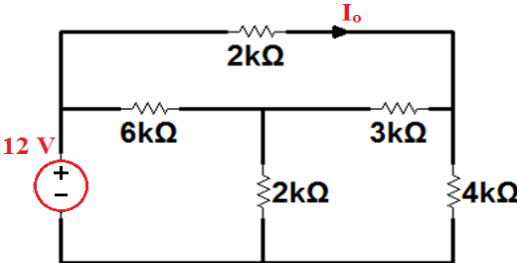
Step 1: Separate the branch through which  $I_0$  is flowing



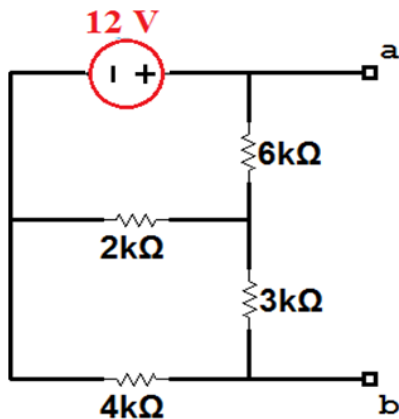Step 2: Find the Norton's equivalent network across the open circuit terminals a-b



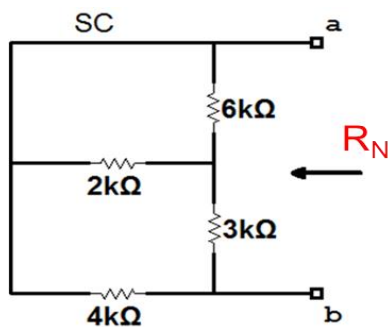
Find the  $R_N$  across the open circuit terminals a-b by short-circuiting 12 V source



$$R_N = [ (6\text{ K} \parallel 2\text{ K}) + 3\text{ K} ] \parallel 4\text{ K}$$

$$\underline{R_N = 2.12\text{ K } \Omega}$$

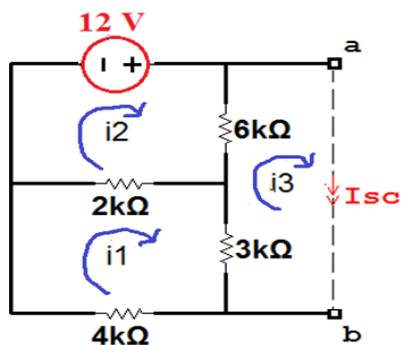Find the  $I_{SC}$  or  $I_N$  through terminals a-b by short-circuiting a-b as shown



By Mesh Analysis:

Mark  $i_1$ ,  $i_2$ ,  $i_3$  as shown

KVL to Mesh 1:

$$4K i_1 + 2K(i_1 - i_2) + 3K(i_1 - i_3) = 0$$

$$9K i_1 - 2K i_2 - 3K i_3 = 0 \dots\dots\dots \text{Eq1}$$

KVL to mesh 2:

$$-12 + 6K(i_2 - i_3) + 2K(i_2 - i_1) = 0$$

$$-2K i_1 + 8K i_2 - 6K i_3 = 12 \dots\dots\dots \text{Eq2}$$

KVL to mesh 3:

$$3K(i_3 - i_1) + 6K(i_3 - i_2) = 0$$


$$-3K i_1 - 6K i_2 + 9K i_3 = 0 \dots\dots\dots \text{Eq3}$$

Solving Eq1, Eq2 and Eq3 we have,



$$i_1 = 3\text{mA}, \quad i_2 = 6\text{mA}, \quad i_3 = 5\text{mA}$$

$$\underline{I_{sc} = i_3 = 5\text{mA}}$$

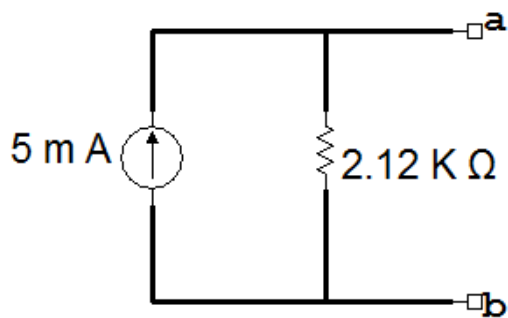Therefore the Norton's equivalent circuit across terminals a-b is



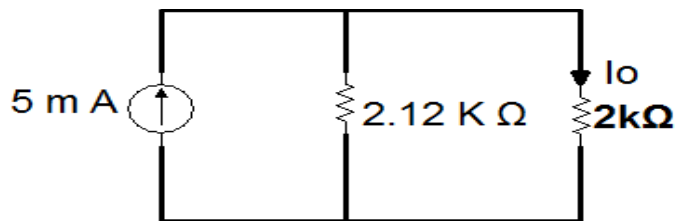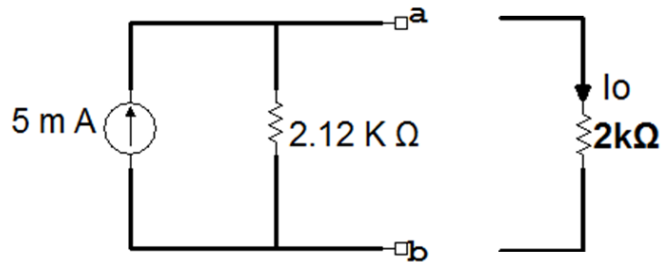
Step 3: Connect the branch separated, back to the Norton's equivalent circuit to find  $I_0$



By Current Division Method

$$I_o = \frac{5\text{ m} \times 2.12\text{ K}}{2\text{ K} + 2.12\text{ K}} = 2.57\text{ mA}$$

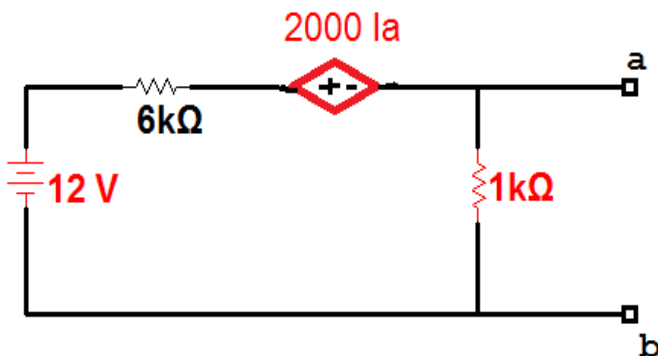P3. Find the Norton's Equivalent network across the terminals a-b




Solution:

Since the network consists of the dependent source (Dependant sources cannot be turned off) the Norton's resistance has to be found out as


$$R_N = V_{oc} / I_{sc}$$

Step 1: To find out  $I_{sc}$  ( $I_N$ )

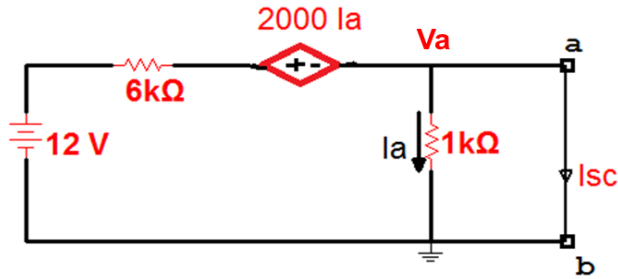Short Circuit the terminals a-b and mark  $I_{sc}$  as shown




$$V_a = I_a = 0$$

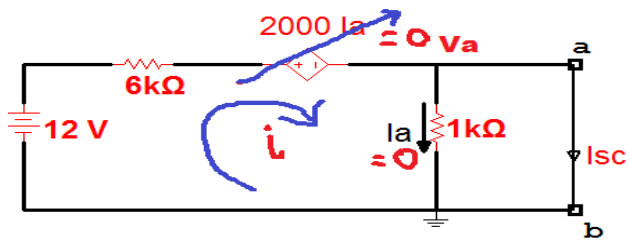

Since  $V_a$  is connected to ground through short circuit terminals a-b  $V_a=0$ .

Hence the circuit gets reduced to...

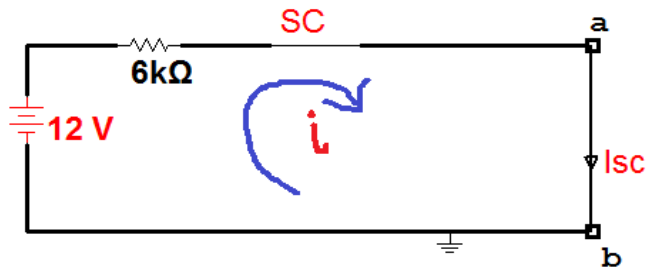


$$\text{KVL: } -12 + 6K i = 0$$

$$i = 12/6K = 2 \text{ m A}$$

$$I_{sc} = i = 2 \text{ m A}$$

Step 2: To find out  $V_{oc}$

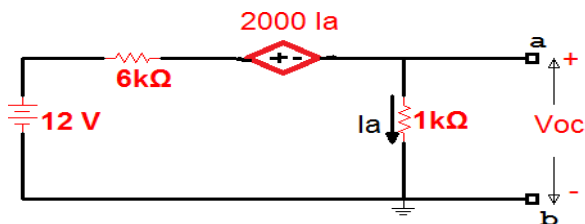



KCL at node a:

$$\frac{V_{oc} + 2000I_a - 12}{6K} + \frac{V_{oc}}{1K} = 0$$


$$2000I_a + 7V_a = 12$$

$$\text{Substituting } I_a = \frac{V_{oc}}{1K}$$

$$V_{oc} = 4/3 \text{ V}$$

$$\text{Therefore } R_N = V_{oc} / I_{sc} = 667 \Omega$$

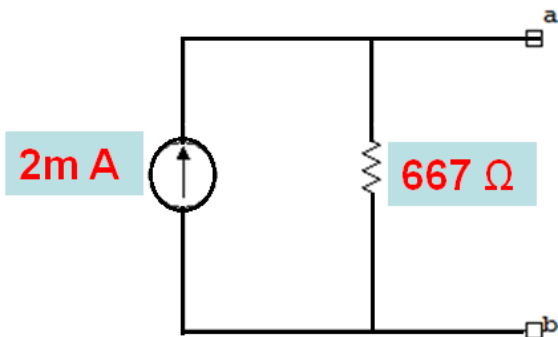Therefore Norton's equivalent circuit across the terminals a-b is given by



## Theorem 2: Thevenin's Theorem


Definition :

Thevenin's Theorem states that a linear two terminal network can be replaced by an equivalent network consisting of an Voltage  $V_T$  in series with a resistor  $R_T$  , where

- $R_T$  is the equivalent resistance at the terminals when the independent sources are turned off
- $V_T$  is open circuit voltage across the terminals.

If the circuit consists of the dependent sources the Norton's resistance has to be found out as  $R_T = V_{oc} / I_{sc}$

P1. Find  $V_O$  by Thevenin's Theorem

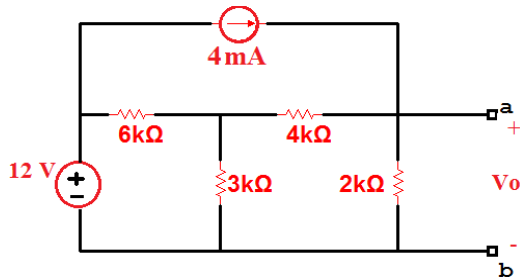


Solution:

Step 1: Remove resistor  $2K \Omega$  from the circuit across which  $V_O$  is dropping


Step 2: Find the Thevenin's network across the open circuit terminals a-b

Step 3: Connect  $2K \Omega$  (Disconnected in Step 1) across the open circuit terminals a-b and find  $V_O$ .


Circuit can be visualized as,

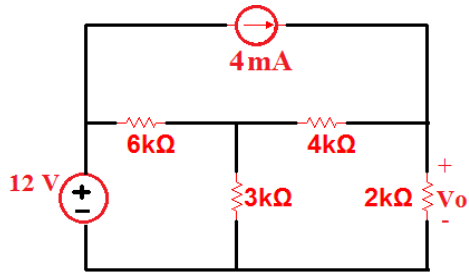

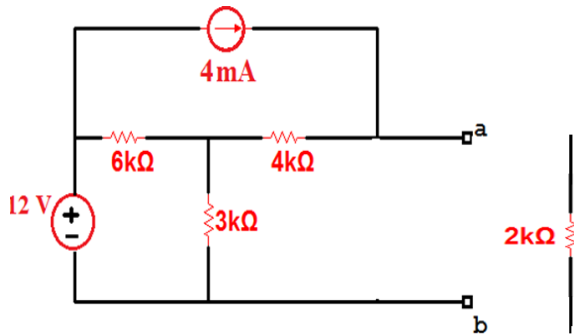Step 1: Remove resistor  $2\text{k}\Omega$  from the circuit across which  $V_O$  is dropping and mark terminals a-b




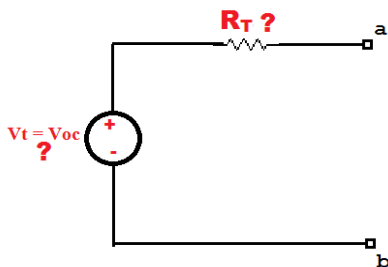Step 2: Find the Thevenin's network across the open circuit terminals a-b



To find  $V_{OC}$ :

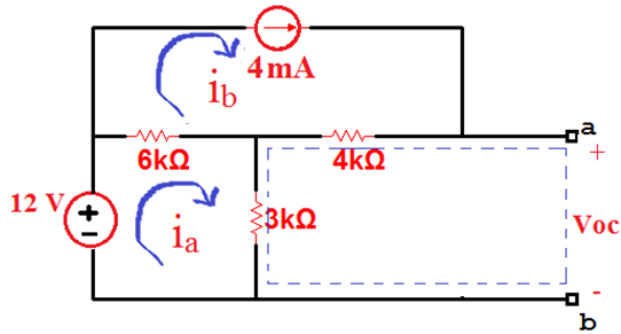Mark  $V_{OC}$  across the open circuit terminals as shown:



Mark Mesh currents  $i_a$  and  $i_b$ :

By Observation:

$$I_a = 4 \text{ mA}$$

Applying KVL to Mesh 1:

$$-12 + 6K(i_a - i_b) + 3K i_a = 0$$

$$9K i_a - 6K i_b = 12$$

$$\text{Sub. } I_a = 4 \text{ mA,}$$

$$I_b = 4 \text{ mA}$$

To find  $V_{oc}$  apply KVL along the dotted path:


$$-3K I_a - 4K I_b + V_{oc} = 0$$

Sub.  $I_a$  and  $I_b$ ,

$$V_{oc} = 28 \text{ V}$$

To find  $R_T$  :


Deactivate the independent sources

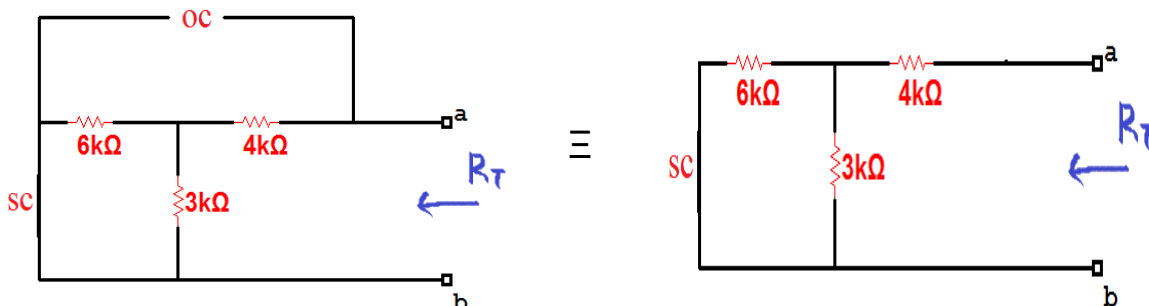

$$R_T = (6K \parallel 3K) + 4K$$


$$R_T = 6K$$

Therefore the Thevenini's network is

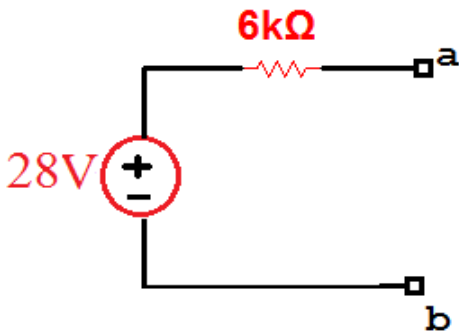

Step 3: To find  $V_O$

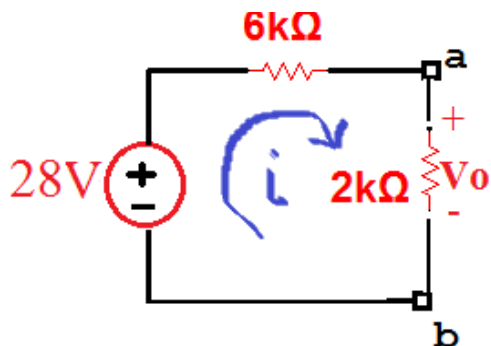Now connect 2 K  $\Omega$  across a-b to find  $V_O$




KVL gives,

$$-28 + 6K i + 2K i = 0$$

$$i = 28/8K = 3.5 \text{ mA}$$

$$V_O = 2K i = 7 \text{ V}$$

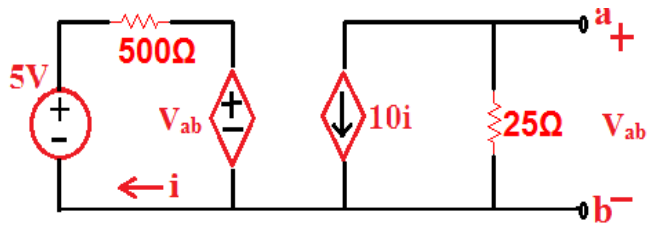P2. Find the Thevenin's Equivalent circuit across terminals a-b




Solution:

Since the dependant sources are involved  $R_T$  is given by

$$R_T = V_{oc} / I_{SC}$$

Step 1: To find  $V_{OC}$

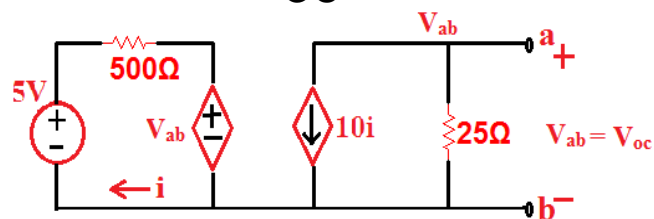

Applying KVL to LHS part:

$$-5 + 500i + V_{ab} = 0$$

$$500i + V_{ab} = 5$$

Applying KCL to RHS part:

$$10i + V_{ab} / 25 = 0$$


$$250i + V_{ab} = 0$$

Solving equations we have

$i = 0.02 \text{ A}$	$V_{ab} = -5 \text{ V}$
----------------------	-------------------------

$V_{oc} = V_{ab} = -5 \text{ V}$
----------------------------------

Step 2: To find  $I_{SC}$

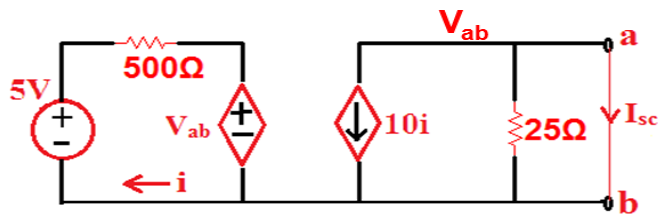


Short circuit terminals a-b and mark  $I_{SC}$  as shown

Mark  $V_{ab}$

Since  $V_{ab}$  is connected to ground through a-b,  $V_{ab} = 0$

Since  $25\ \Omega$  is in parallel with a short,  $25\ \Omega$  is redundant

Therefore the circuit reduces to,

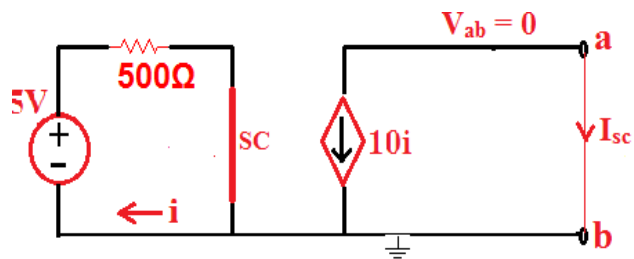

From LHS part, KVL gives

$$-5 + 500i = 0$$

From RHS part,

$$I_{SC} = -10i$$


and sub.  $i = 0.01\text{ A}$

$$I_{SC} = -0.1\text{ A}$$


Therefore  $R_T = V_{OC} / I_{SC} = -5 / -0.1$

$$R_T = 50 \Omega$$

Therefore the Thevenin's network is,

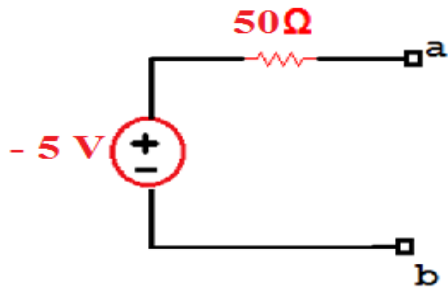

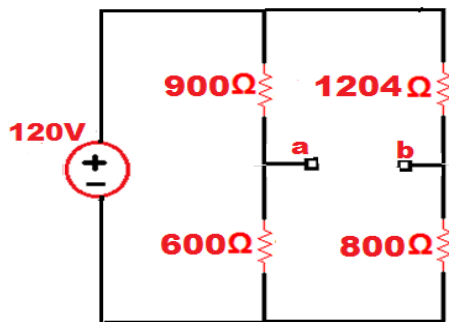
P3. Find the Thevenin's Equivalent network across terminals a-b



Solution:

Step1: To find Mark  $V_{OC}$  ( $V_T$ ) across terminals a-b

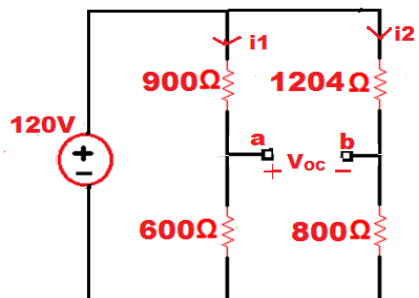Mark the branch currents  $i_1$  and  $i_2$  as shown





Applying KVL to mesh 1

$$-120 + 900 i_1 + 600 i_1 = 0$$


$$i_1 = 0.08 \text{ A}$$

Applying KVL to mesh 2

$$-120 + 1204 i_2 + 800 i_2 = 0$$

$$i_2 = 0.05988 \text{ A}$$

To find  $V_{OC}$ :

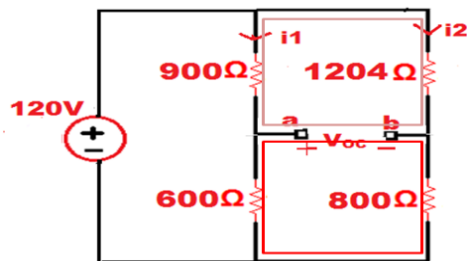


Applying KVL along the pink path

$$-900 i_1 + 1204 i_2 - V_{OC} = 0$$


$$V_{OC} = 0.095 \text{ V}$$

Step 2: To find  $R_T$

Turning off 120 V source

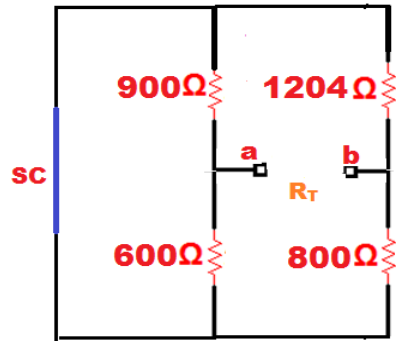


which can be visualized as

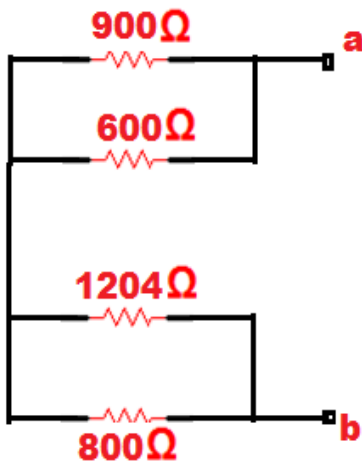

$$R_T = (900 \parallel 600) + (1204 \parallel 800)$$

$$R_T = 840.638 \Omega$$

Therefore Thevenin's network is

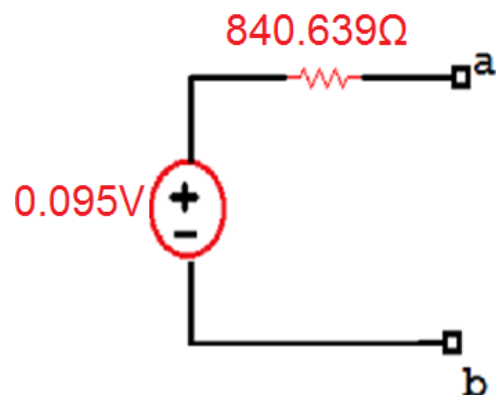

Summary:


1. Thevenin's network is a Voltage in series with a resistor
2. Thevenin's voltage is  $V_{OC}$  across the terminals
3. Thevenin's resistance and Norton's resistance are the same.
4. Thevenin's and Norton's equivalent networks can be obtained by source transformation.

### Theorem 3: Maximum Power Transfer Theorem

There are three cases to be considered in this

1. AC circuits with Impedance ( $Z_L$ ) as load
2. AC circuits with purely resistive load ( $R_L$ )
3. DC circuits with resistive load ( $R_L$ )


Conditions for Maximum Power Transfer :

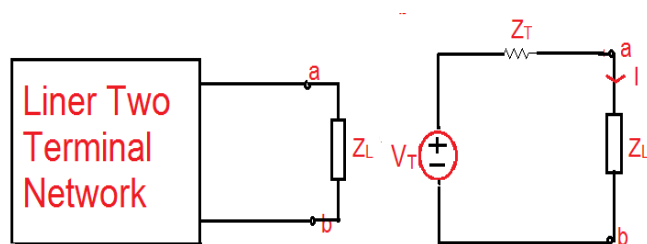

where,

$$Z_T = R_T + j X_T$$

$$Z_L = R_L + j X_L$$

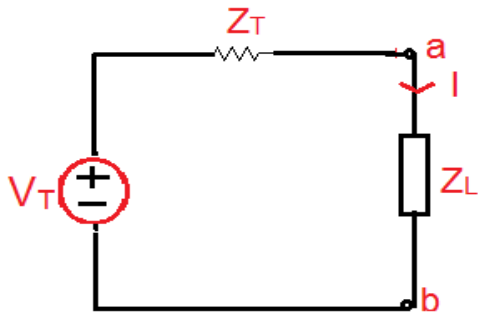

KVL to closed path:

$$-V_T + Z_T I + Z_L I = 0$$

$$I = \frac{V_T}{Z_T + Z_L} = \frac{V_T}{(R_T + jX_T) + (R_L + jX_L)}$$

The average power delivered to the load is

$$P = \frac{1}{2} |I|^2 R \quad \dots\dots\dots \textcircled{1}$$

$$I^2 = \frac{V_T^2}{[(R_T + jX_T) + (R_L + jX_L)]^2}$$

$$I^2 = \frac{V_T^2}{[(R_T + R_L) + j(X_T + X_L)]^2}$$

$$|I|^2 = \frac{|V_T|^2}{[\sqrt{(R_T + R_L)^2 + (X_T + X_L)^2}]^2}$$

Substituting in equation in 1

$$P = \frac{R_L}{2} \frac{|V_T|^2}{(R_T + R_L)^2 + (X_T + X_L)^2}$$

For this P to be  $P_{Max}$  we can vary two parameters

–  $R_L$  and  $X_L$  in the load impedance.

Mathematically it can be done by differentiating  $P$  with respect to  $R_L$  and  $X_L$  partially and equating it to zero respectively.

i.e,

$$\frac{\partial P}{\partial R_L} = 0 \quad \text{and} \quad \frac{\partial P}{\partial X_L} = 0$$

Performing  $\frac{\partial P}{\partial R_L} = 0$  results in

$$(R_T + R_L)^2 + (X_T + X_L)^2 - 2R_L(R_T + R_L) = 0$$

This implies

$$R_L = \sqrt{R_T^2 + (X_T + X_L)^2} \quad \dots\dots\dots (2)$$

Performing  $\frac{\partial P}{\partial X_L} = 0$  results in

$$X_L = -X_T \quad \dots\dots\dots (3)$$

Substituting (3) in (2)

$$R_L = R_T \quad \dots\dots\dots (4)$$

From equations 3 and 4

$$Z_L = R_L + j X_L = R_T - j X_T$$

$$Z_L = Z_T^*$$

If the Load  $Z_L$  is purely resistive then

$$X_L = 0 \text{ and } Z_L = R_L$$

Substituting  $X_L = 0$  in 2


$$R_L = \sqrt{R_T^2 + X_T^2} \dots\dots\dots 5$$

$$R_L = |Z_T| \dots\dots\dots 6$$

Equations 4 , 5 and 6 are the conditions for which the maximum power would be transferred to the load.


Highlights:

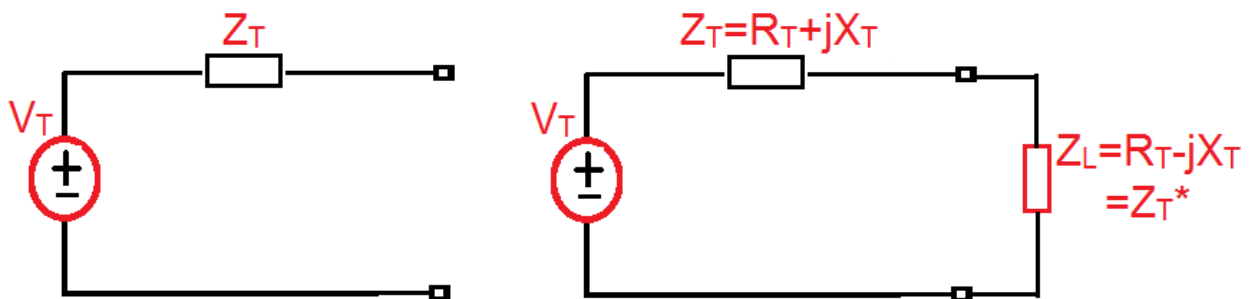1. AC circuits with Impedance ( $Z_L$ ) as load




$$P_{\max} = |i|^2 R_L$$

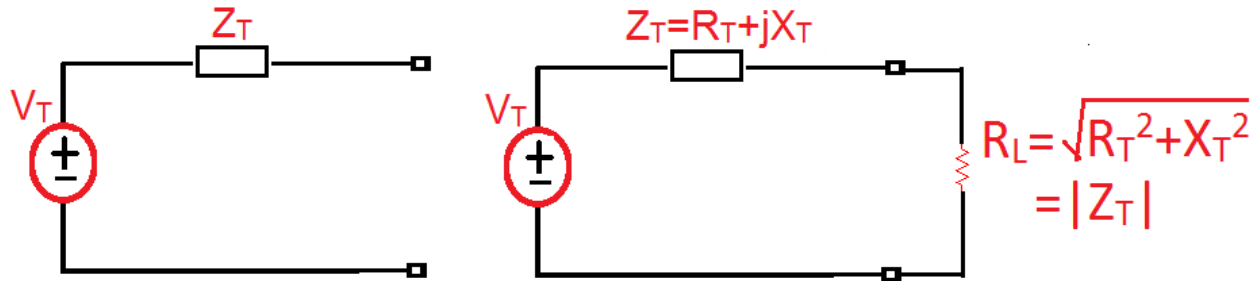2. AC circuits with Pure Resistive ( $R_L$ ) load




$$P_{\max} = |i|^2 R_L$$

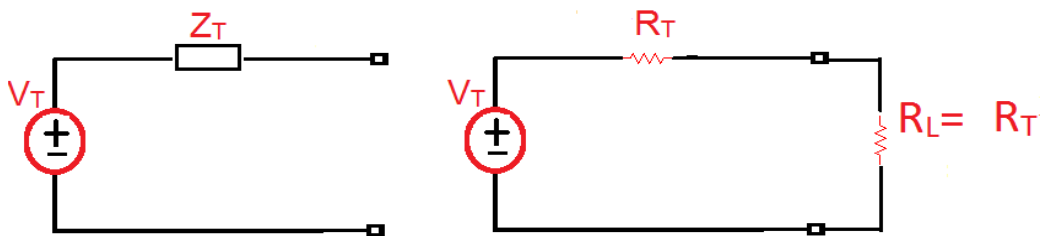3. DC circuits with Resistor ( $R_L$ ) as the load



$$P_{\max} = i^2 R_L$$

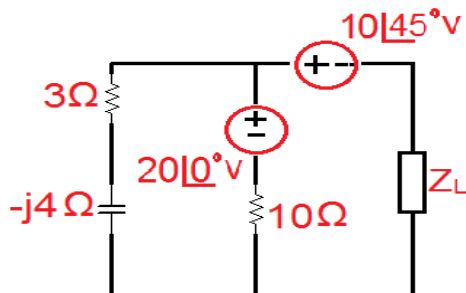P1. Calculate the value of  $Z_L$  for maximum power transfer and also calculate the maximum power.



Solution:


Step1. Remove the Impedance  $Z_L$

Step2. Find the Thevenin's equivalent network across the terminals a-b

Step3. Connect  $Z_L = Z_T^*$  across the terminals a-b for the maximum power transfer.

Step4. Find  $P_{\max} = |I|^2 R_L$

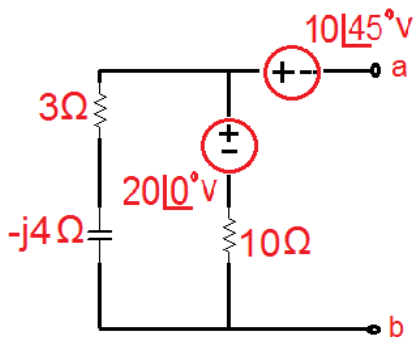
Step1. Remove the Impedance  $Z_L$  and mark terminals a-b



Step2. Find the Thevenin's equivalent network across the terminals a-b.

To find Thevenin's Impedance  $Z_T$ :

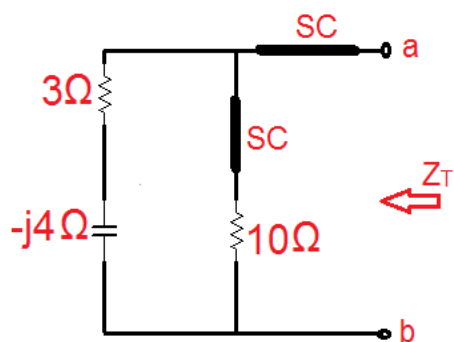Deactivating the independent sources we have,





$$Z_T = 10 \parallel (3 - j4)$$

$$Z_T = 2.97 - j 2.16 \Omega$$

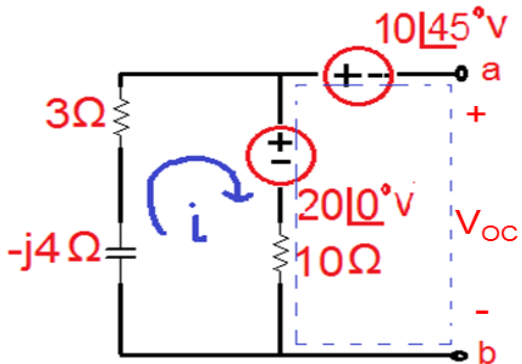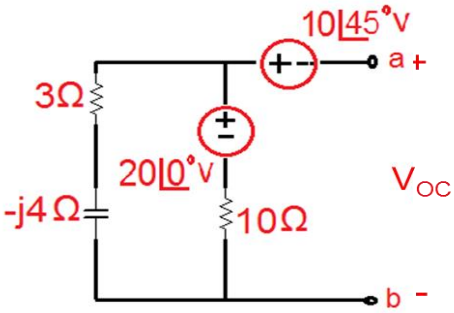To find Thevenin's Voltage  $V_T$  or  $V_{OC}$ :





KVL implies:

$$(3-j4)i + 20 + 10i = 0$$

$$i = -1.405 - j0.432$$

KVL along the dotted path to find  $V_{OC}$ :


$$-10i - 20 + 10\angle 45 + V_{OC} = 0$$

Substituting  $i$


$$V_T = -1.121 - j1.391$$

$$= 11.44 \angle -95.62^\circ \text{ V}$$

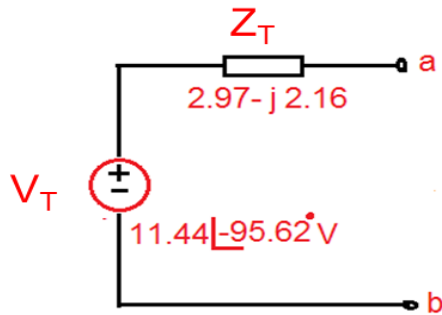Therefore Thevenin's equivalent network is



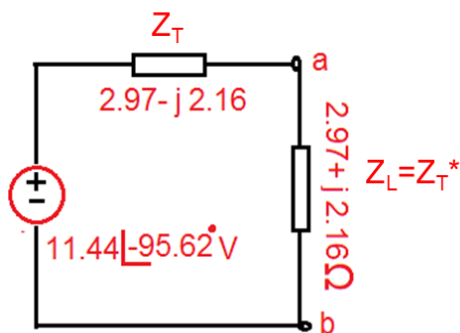Step 3. Connect  $Z_L = Z_T^*$  across the terminals a-b to find the maximum power transfer.



KVL implies:

$$-11.44 \angle -95.62^\circ + (2.9729)i + (2.9729)i = 0$$

$$i = -0.185 - j 1.916 \text{ A}$$

$$i = 1.925 \angle -95.62^\circ \text{ A}$$


Step 4. To find  $P_{\max}$

$$P_{\max} = |i|^2 R_L$$

$$= (1.925)^2 \times 2.9729$$

$$P_{\max} = 11 \text{ Watts}$$

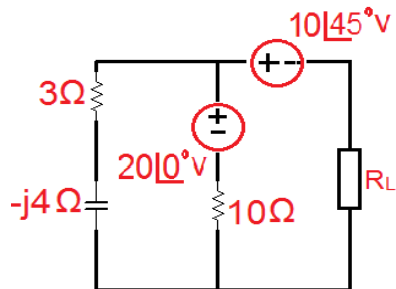P2. Calculate the value of  $R_L$  for maximum power transfer and also calculate the maximum power.



Solution:


Step1. Remove the Impedance  $Z_L$

Step2. Find the Thevenin's equivalent network across the terminals a-b

Step3. Connect  $Z_L = |Z|$  across the terminals a-b for the maximum power transfer.

Step4. Find  $P_{\max} = |I|^2 R_L$

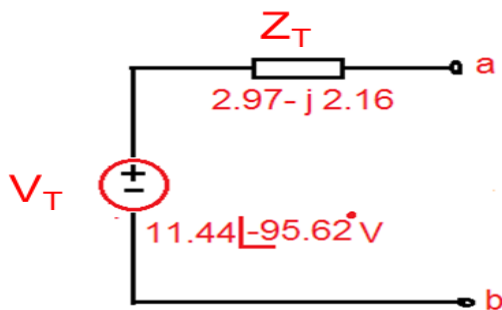
From Step1 and Step2 (Refer P1), the Thevenin's equivalent is



Step3. Connect  $R_L = |Z|$  across the terminals a-b to find the maximum power transfer.

$$R_L = |Z_T| = \sqrt{(2.97)^2 + (2.16)^2}$$

$$R_L = 3.675 \Omega$$

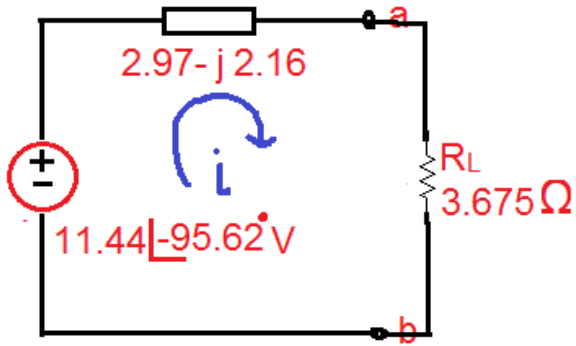

KVL implies

$$-11.44 \angle -95.62 + (2.97 - j 2.16) i + 3.675 i = 0$$

$$i = 1.6377 \angle -77.62 \text{ A}$$


Step 4. To find  $P_{\max}$

$$P_{\max} = | i |^2 R_L$$

$$= (1.6377)^2 \times 3.675$$


$$P_{\max} = 9.85 \text{ W}$$

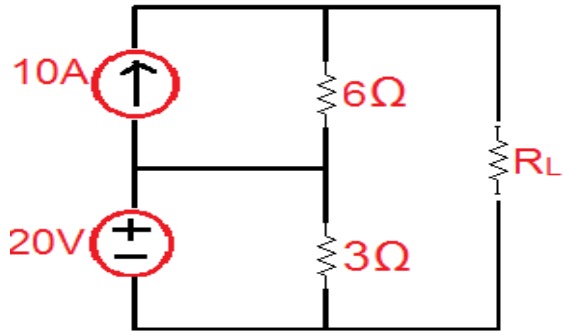P3. Find the  $R_L$  across the load for which maximum power will be transferred to the load and hence find the maximum power




Solution:

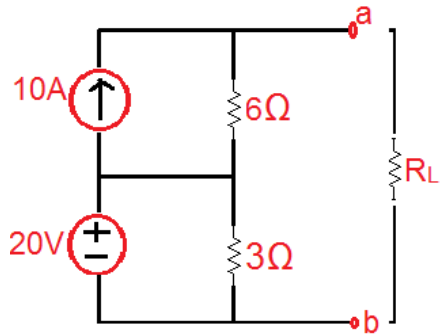Step 1: Remove the resistor  $R_L$  and mark terminals a-b as shown



Step 2: Find the Thevenin's network across the terminals a-b

To find  $V_{oc}$ :

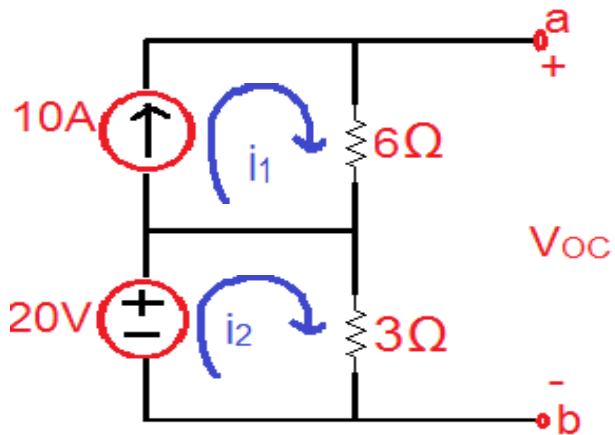


By observation:

$$i_1 = 10 \text{ A}$$

KVL to mesh 2:

$$-20 + 3 i_2 = 0$$

$$i_2 = 20/3 \text{ A}$$

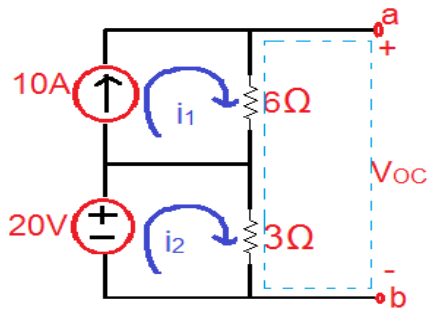

$$- 3i_2 - 6i_1 + V_{oc} = 0$$


KVL along the dotted path

$$V_{oc} = 6 i_1 + 3 i_2$$


Substituting  $i_1$  and  $i_2$

$$V_T = V_{oc} = 80 \text{ V}$$

To find  $R_T$ :

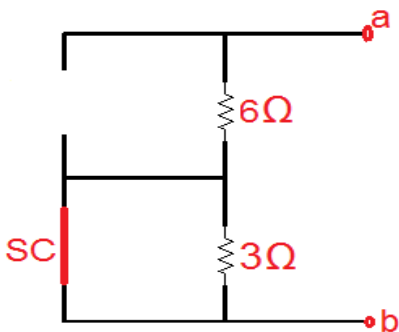


which can be visualized as

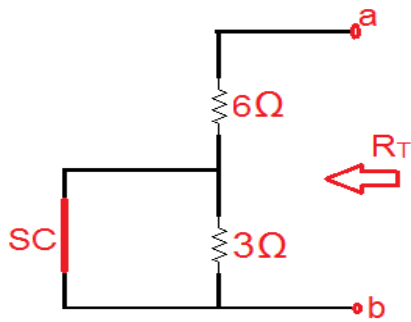

Since  $3\ \Omega$  is in parallel with the short, it is redundant.


Therefore  $R_T = 6\ \Omega$

Therefore Thevenin's network is

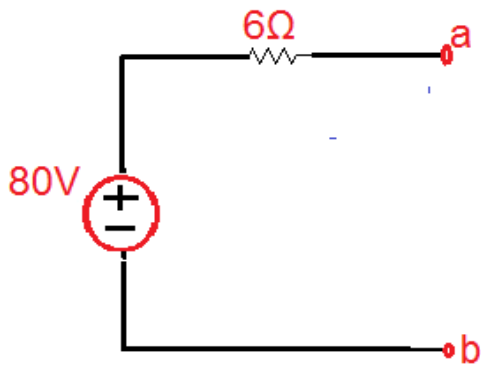

Step 3: To find  $P_{\max}$

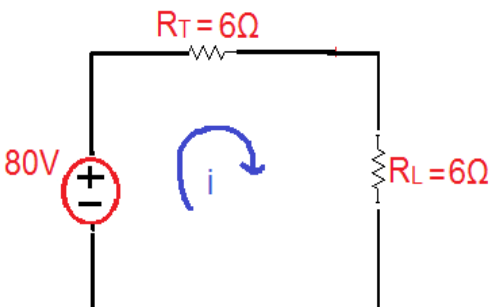Connect  $R_L = R_T$  across the terminals a-b



KVL implies:

$$-80 + 6i + 6i = 0$$

$$i = 20/3 \text{ A}$$

$$P_{\max} = i^2 R_L = (20/3)^2 \times 6 = 266.66 \text{ W}$$

Summary:

1. Maximum power transfer theorem is the extension of Thevenin's theorem.
2. The conditions for Maximum power to be transferred to the load are
  - i) For AC circuits if load is impedance then  $Z_L = Z_T^*$
  - ii) For AC circuits if load is purely resistive then  $R_L = |Z_T|$
  - iii) For DC circuits  $R_L = R_T$
3. Power is always a real entity and therefore for power calculations always real part of  $Z_L$  (i.e.,  $R_L$ ) is used.




## Theorem 4: Superposition Theorem

### Statement:

In any Linear circuit containing multiple independent sources, a current or a voltage at any point in the circuit can be calculated as algebraic sum of Individual contributions of each source when acting alone.
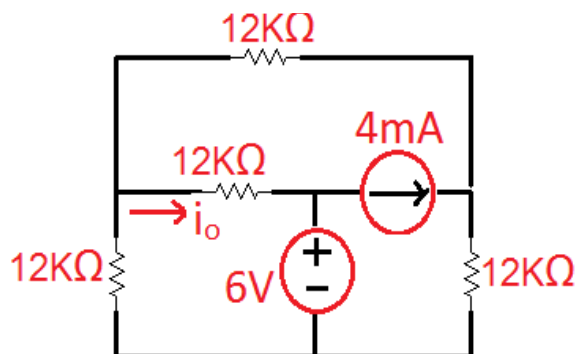
### Problems:

P1. Find  $i_o$  by Super position theorem.



Solution:

$$\text{Let } i_o = i_{o1} + i_{o2}$$

where,



$i_{o1}$  is the contribution of 6 V source when acting alone and

$i_{o2}$  is the contribution of 4mA source when acting alone

Steps:

Step 1 : To find  $i_{o1}$  which is the contribution of 6 V acting alone

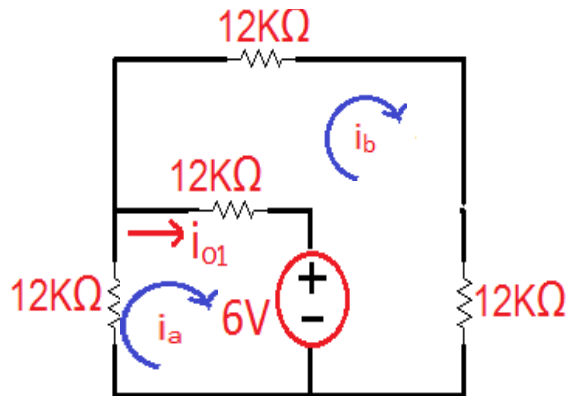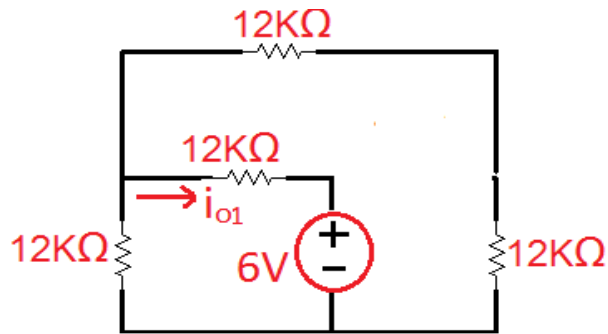Deactivating the 4mA source the circuit becomes



Applying KVL to mesh 1:

$$12K i_a + 12K (i_a - i_b) + 6 = 0$$

$$24K i_a - 12K i_b = -6 \dots\dots\dots \text{Eq1}$$

Applying KVL to mesh 2:

$$12K (i_b - i_a) + 12K i_b + 12K i_b - 6 = 0$$

$$-12K i_a + 36K i_b = 6 \dots\dots\dots \text{Eq2}$$

Solving equations Eq1 and Eq2,


$$i_a = -0.2 \text{ mA}$$

$$i_b = 0.1 \text{ mA}$$

$$\mathbf{i_{o1} = i_a - i_b = -0.3 \text{ mA}}$$

Step 2 : To find  $i_{o2}$  which is the contribution of  $4\text{mA}$  source acting alone

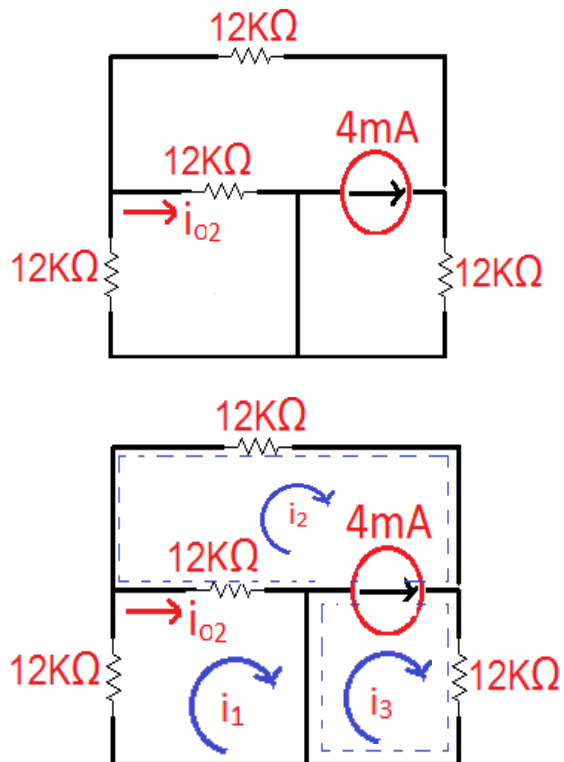Deactivating the  $6\text{V}$  source the circuit becomes



Constraint equation:

$$i_3 - i_2 = 4\text{mA}$$

Applying KVL to mesh 1:

$$12\text{K} i_1 + 12\text{K} (i_1 - i_2) = 0$$

$$24\text{K} i_1 - 12\text{K} i_2 = 0$$

Applying KVL to Supermesh:

$$12\text{K} (i_2 - i_1) + 12\text{K} i_2 + 12\text{K} i_3 = 0$$

$$-12\text{K} i_1 + 24\text{K} i_2 + 12\text{K} i_3 = 0$$

Applying KVL to mesh 1:

$$12K i_1 + 12K (i_1 - i_2) = 0$$

$$24K i_1 - 12K i_2 = 0$$

Solving equations 1, 2 and 3

$$i_1 = -0.8 \text{ mA}; \quad i_2 = -1.6 \text{ mA}; \quad i_3 = 2.4 \text{ mA}$$

$$i_{o2} = i_1 - i_2 = \mathbf{0.8 \text{ mA}}$$

Step 3 : To find  $i_o$


By Super Position Theorem,

$$i_o = i_{o1} + i_{o2}$$

$$i_o = -0.3 \text{ m} + 0.8 \text{ m}$$

$$i_o = \mathbf{0.5 \text{ m A}}$$

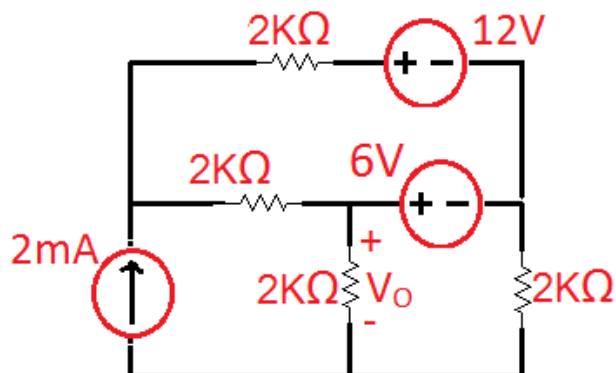P2. Find  $V_o$  by Super position theorem.



Solution:

$$\text{Let } V_0 = V_{01} + V_{02} + V_{03}$$

where,


$V_{01}$  is the contribution of 12V source when acting alone

$V_{02}$  is the contribution of 6V source when acting alone

$V_{03}$  is the contribution of 2mA source when acting alone

Step 1: To find  $V_{01}$

Deactivate 6V and 2mA sources

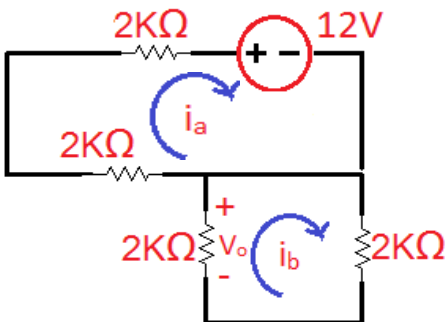

KVL to mesh2:


$$2K i_b + 2K i_b = 0$$

$$i_b = 0$$

$$V_{01} = -2K i_b = 0V$$

Step 2: To find  $V_{02}$

Deactivate 12V and 2mA sources

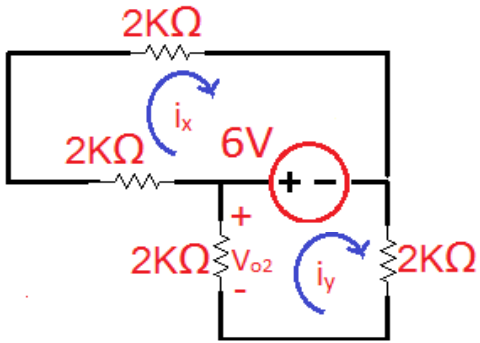

KVL to mesh2:



$$2K i_y + 6 + 2K i_y = 0$$

$$i_y = -1.5\text{mA}$$

$$V_{O2} = -2K i_y = 3\text{V}$$

Step 3: To find  $V_{o3}$

Deactivate 12V and 6V sources

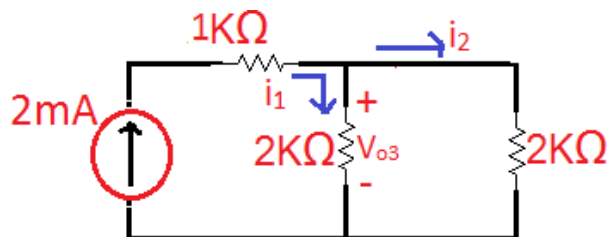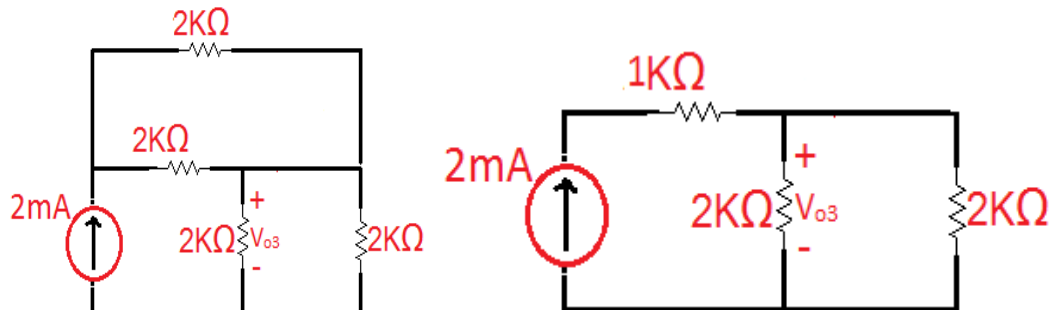

$$i_1 = i_2 = 1\text{mA}$$

$$V_{O3} = 2K i_1 = 2\text{V}$$

Step 4:


By Super position Theorem

$$V_0 = V_{01} + V_{02} + V_{03}$$

$$V_0 = 0 + 3 + 2$$

$$V_0 = 5 \text{ V}$$

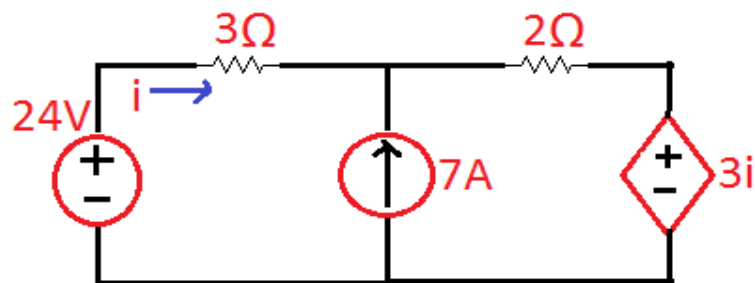P3. Find  $i$  by Super position theorem.



Solution:

$$\text{Let } i = i_1 + i_2$$

where,


$i_1$  is the contribution of 24V source when acting alone

$i_2$  is the contribution of 7A source when acting alone

The dependant voltage source cannot be deactivated - keep it as it is.

Step 1: To find  $i_1$

Deactivate 7A source

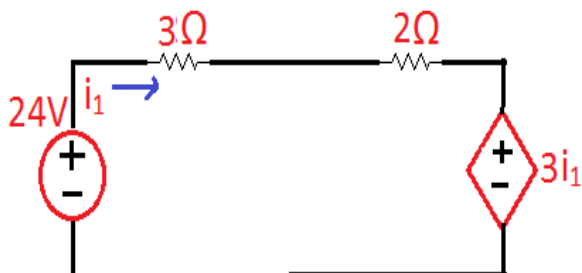



Applying KVL:

$$-24 + 3 i_1 + 2 i_1 + 3 i_1 = 0$$

$$i_1 = 3 \text{ A}$$

Step 2: To find  $i_2$

Deactivate 24V source

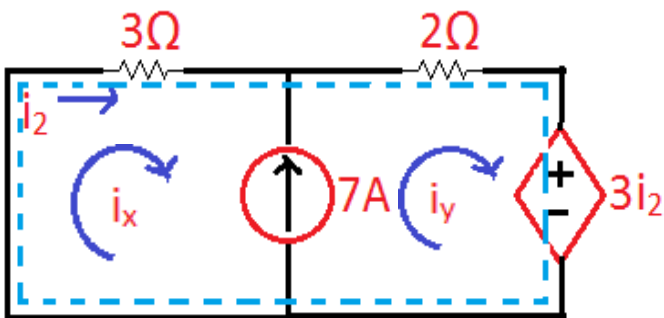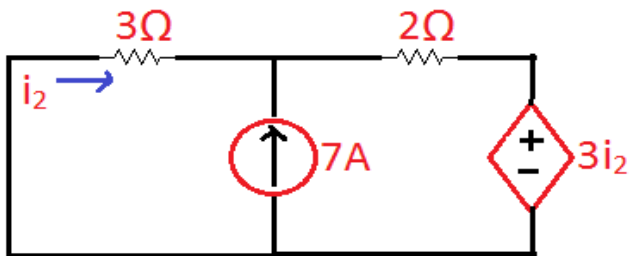

Constraint equation:

$$-i_x + i_y = 7\text{A}$$

KVL to Supermesh:

$$3 i_x + 2 i_y + 3 i_2 = 0$$

Sub.  $i_2 = i_x$

$$3 i_x + 2 i_y + 3 i_x = 0$$

$$6 i_x + 2 i_y = 0$$

Solving the equations

$$-i_x + i_y = 7\text{A}$$



$$6 i_x + 2 i_y = 0$$

Implies,

$$i_x = -1.75 \text{ A and } i_y = 5.25 \text{ A}$$

$$i_2 = i_x = -1.75 \text{ A}$$

Step 3:

By Super position Theorem

$$i = i_1 + i_2$$

$$i = 3 - 1.75$$

$$i = 1.25 \text{ A}$$

Summary:

1. Superposition theorem is applicable to circuits with multiple independent sources only.
2. Dependant sources can be present.
3. At a time only one independent source should be acting, which gives its individual contribution.
4. Algebraic summation of the individual contributions gives the actual current/voltage in a circuit.
5. It is as good as cutting down complex problems into simpler ones.


## Theorem 5: Reciprocity Theorem

### Statement:

In any Linear Bilateral single source circuit, the ratio of Excitation to Response is constant when the positions of Excitation and Response are interchanged.

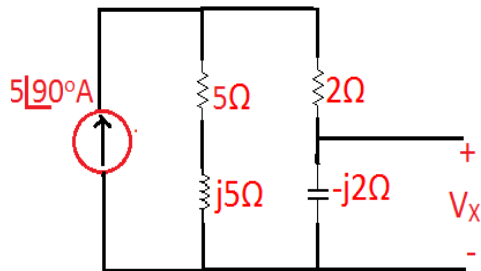
### Problems:

P1. Find  $V_x$  and verify Reciprocity theorem.



### Solution:

Step 1: To find the response  $V_x$

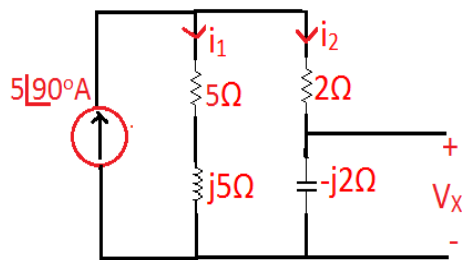

Mark the branch currents  $i_1$  and  $i_2$

By current Division Rule:

$$i_2 = \frac{(5 + j5)5\angle 90}{(5 + j5) + (2 - j2)}$$


$$i_2 = -1.72 + j4.13 = 4.64 \angle 111.8$$

Therefore  $V_x$  is given by,


$$V_x = (-j2)i_2$$

$$V_x = 8.62 + j3.44 = 9.28 \angle 21.8^\circ \text{V}$$

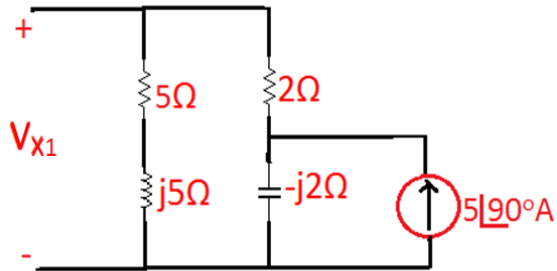Step 2: Interchange the Excitation and Response



To find  $V_{x1}$  :

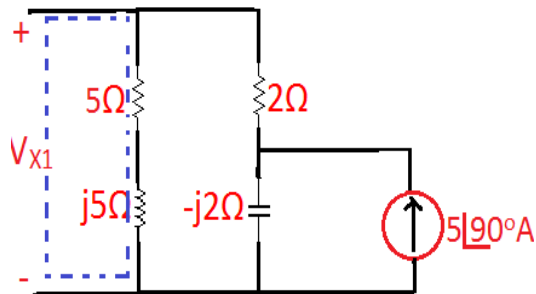

By Observation:

$$i_2 = -5 \angle 90^\circ \text{A}$$

KVL to Mesh1:

$$(5+j5)i_1 + 2i_1 - j2(i_1 - i_2) = 0$$

Sub.

$$i_2 = -5 \angle 90^\circ \text{A}$$

$$i_1 = -1.2 + j 0.5 = 1.31 \angle 156.8^\circ \text{A}$$

KVL along the dotted path:


$$-V_{x1} - (5+j5) i_1 = 0$$

$$\text{Sub. } i_1 = 1.31 \angle 156.8^\circ$$

$$V_{x1} = 9.28 \angle 21.8^\circ \text{V}$$


Since  $V_x = V_{x1}$ , Reciprocity Theorem is Verified .

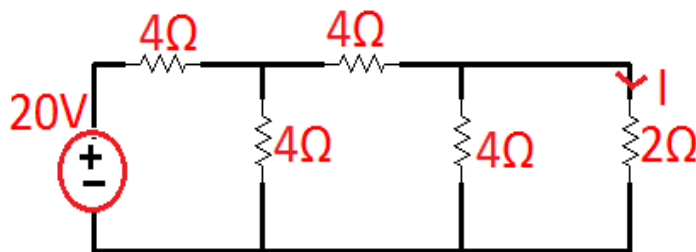P2. Find I and verify Reciprocity theorem.



Solution:

Step 1: To find the response I

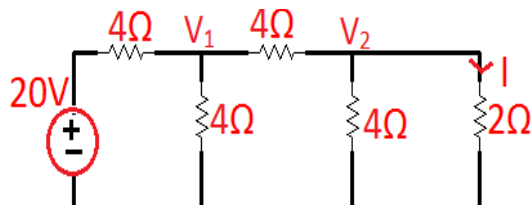

KCL at node 1:

$$\frac{V_1 - 20}{4} + \frac{V_1}{4} + \frac{V_1 - V_2}{4} = 0$$

$$\frac{V_1 - 20 + V_1 + V_1 - V_2}{4} = 0$$

$$3V_1 - V_2 = 20 \dots\dots\dots \text{Eq1}$$

KCL at node 2:

$$\frac{V_2}{4} + \frac{V_2 - V_1}{4} + \frac{V_2}{2} = 0$$

$$\frac{V_2 + V_2 - V_1 + 2V_2}{4} = 0$$

$$-V_1 + 4V_2 = 0 \dots\dots\dots \text{Eq2}$$


Solving equations 1 and 2

$$V_1 = 7.27 \text{ V} ; V_2 = 1.8181 \text{ V}$$

$$I = \frac{V_2}{2} = 0.909 \text{ A}$$

Step 2: To find the response  $I'$

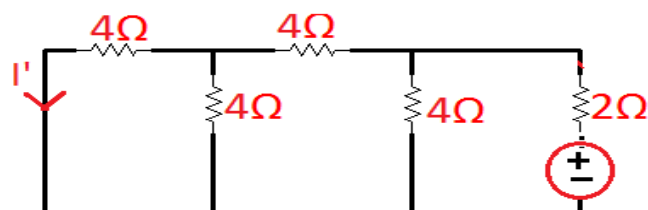Interchange the positions of Excitation and Response



KCL at node 1:

$$\frac{V_1}{4} + \frac{V_1}{4} + \frac{V_1 - V_2}{4} = 0$$

$$\frac{V_1 + V_1 + V_1 - V_2}{4} = 0$$

$$3V_1 - V_2 = 0 \text{ -----Eq A}$$

KCL at node 2:

$$\frac{V_2 - V_1}{4} + \frac{V_2}{4} + \frac{V_2 - 20}{2} = 0$$

$$\frac{V_2 - V_1 + V_2 + 2V_2 - 40}{4} = 0$$

$$-V_1 + 4V_2 = 40 \text{ .....Eq B}$$


Solving equations 1 and 2

$$V_1 = 3.6363 \text{ V ; } V_2 = 10.9 \text{ V}$$

$$I' = \frac{V_1}{4} = 0.909 \text{ A}$$


Since  $I = I'$ , Reciprocity Theorem is Verified.

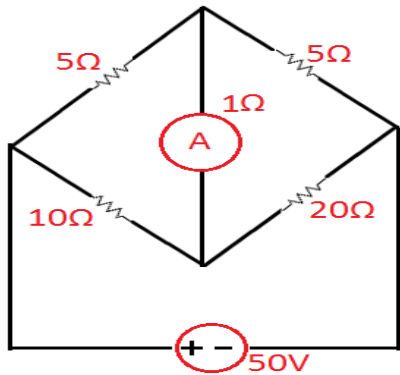P3. Find The current through the ammeter and verify Reciprocity theorem.



Solution:

Step 1: To find the Ammeter current

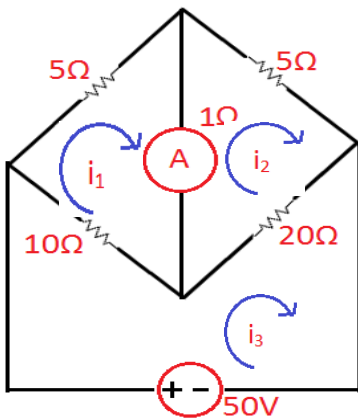

KVL at mesh 1:

$$5 i_1 + 1 (i_1 - i_2) + 10 (i_1 - i_3) = 0$$

KVL at mesh 2:

$$1 (i_2 - i_1) + 5 i_2 + 20 (i_2 - i_3) = 0$$

KVL at mesh 3:

$$10 (i_3 - i_1) + 20 (i_3 - i_2) - 50 = 0$$

Which give,

$$16 i_1 - i_2 + 10 i_3 = 0$$

$$-i_1 + 26 i_2 - 20 i_3 = 0$$

$$-10 i_1 - 20 i_2 + 30 i_3 = 50$$


Solving the above for  $i_1$ ,  $i_2$  and  $i_3$

$$i_1 = 4.59 \text{ A}, i_2 = 5.4098 \text{ A} \text{ and } i_3 = 6.8 \text{ A}$$


$$I_A = i_2 - i_1 = 0.8 \text{ A} \text{ Flowing upwards}$$

Step 2: To find the response  $I_A$

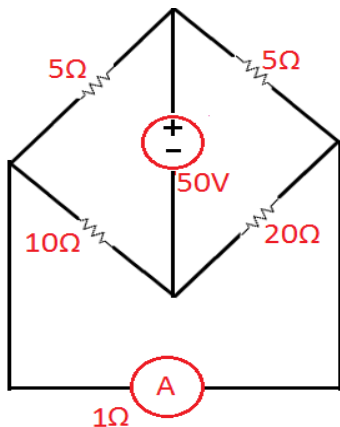Interchange the positions of Excitation and Response





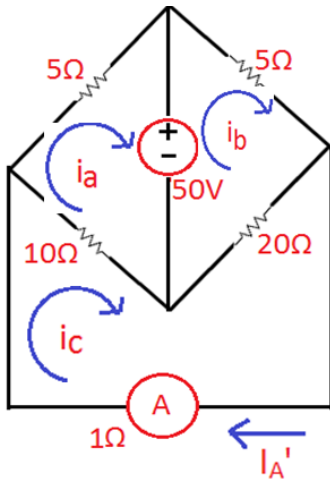

KVL at mesh 1:

$$5 i_a + 50 + 10 (i_a - i_c) = 0$$

KVL at mesh 2:

$$-50 + 5 i_b + 20 (i_b - i_c) = 0$$

KVL at mesh 3:

$$10 (i_c - i_a) + 20 (i_c - i_b) + 1 i_c = 0$$

Which give

$$15 i_a - 10 i_c = -50$$

$$25 i_b - 20 i_c = 50$$

$$-10 i_a - 20 i_b + 31 i_c = 0$$

Solving the above for  $i_a$ ,  $i_b$  and  $i_c$

$$i_a = -2.8 \text{ A}, i_b = 2.64 \text{ A} \text{ and } i_c = 0.8 \text{ A}$$

$$I'A = i_c = 0.8 \text{ A}$$

Since  $I'A = I A$ , Reciprocity Theorem is Verified

### Theorem 6: Millman's Theorem

#### Statement:


If 'n' generators of EMFs  $E_1, E_2, \dots, E_n$  with internal impedances  $Z_1, Z_2, \dots, Z_n$  are connected in parallel then the EMFs and the impedances can be combined to give a single EMF  $E$  with internal Impedance  $Z$ , where

$$E = \frac{E_1 Y_1 + E_2 Y_2 \dots + E_n Y_n}{Y_1 + Y_2 \dots + Y_n}$$

and


$$Z = \frac{1}{Y_1 + Y_2 \dots + Y_n}$$

#### Proof:

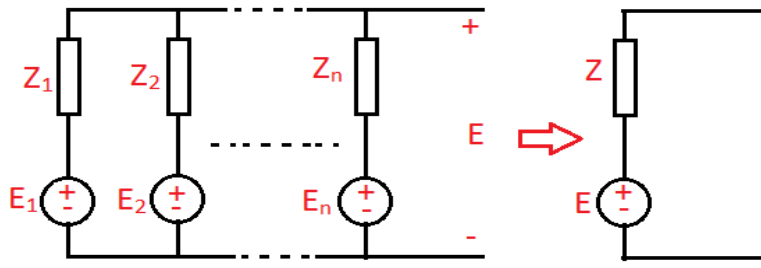

Note that  $Z_1, Z_2, \dots, Z_n$  are the internal impedances

Consider,

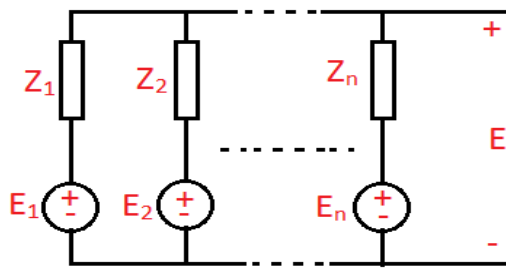

KCL at node E:

$$\frac{E - E_1}{Z_1} + \frac{E - E_2}{Z_2} + \dots + \frac{E - E_n}{Z_n} = 0$$

$$\frac{E - E_1}{Z_1} + \frac{E - E_2}{Z_2} + \dots + \frac{E - E_n}{Z_n} = 0$$

$$E \left[ \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n} \right] = \frac{E_1}{Z_1} + \frac{E_2}{Z_2} + \dots + \frac{E_n}{Z_n}$$

$$E[Y_1 + Y_2 + \dots + Y_n] = E_1 Y_1 + E_2 Y_2 + \dots + E_n Y_n$$

$$E = \frac{E_1 Y_1 + E_2 Y_2 + \dots + E_n Y_n}{Y_1 + Y_2 + \dots + Y_n}$$

Since all the internal impedances are in parallel,


$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} \dots \dots \frac{1}{Z_n}$$

$$Y = Y_1 + Y_2 \dots \dots + Y_n$$


$$Z = \frac{1}{Y_1 + Y_2 \dots \dots + Y_n}$$

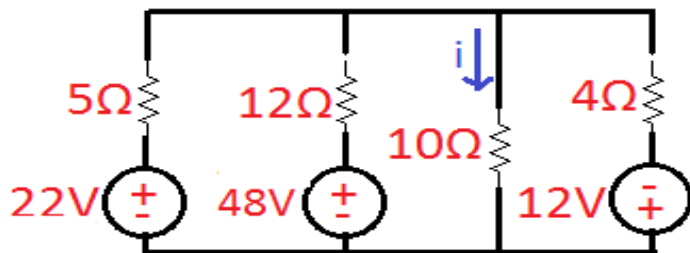
Problems:

P1. Find the current through 10 Ω by Millman's Theorem.




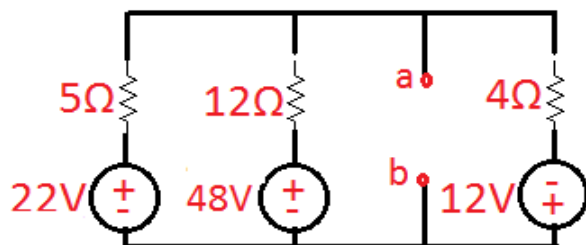Step 1: Remove 10Ω and mark terminals a-b



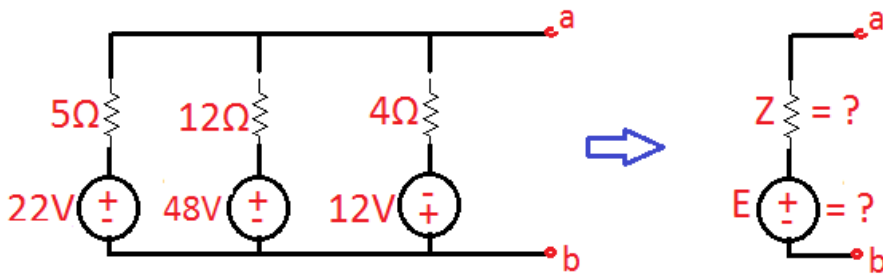

Step 2: To find E and Z

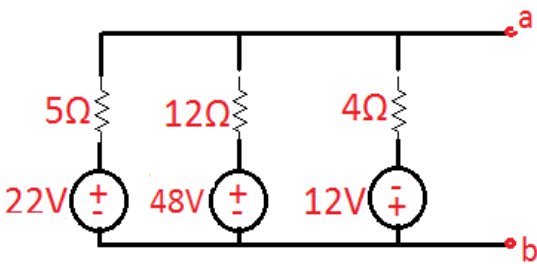

$$E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3}{Y_1 + Y_2 + Y_3}$$

$$E = \frac{22 \left(\frac{1}{5}\right) + 48 \left(\frac{1}{12}\right) - 12 \left(\frac{1}{4}\right)}{\frac{1}{5} + \frac{1}{12} + \frac{1}{4}}$$


$$E = 10.125 \Omega$$

$$Z = \frac{1}{Y_1 + Y_2 + Y_3}$$

$$Z = \frac{1}{\frac{1}{5} + \frac{1}{12} + \frac{1}{4}}$$


$$Z = 1.875 \Omega$$

Therefore by Millman's Theorem

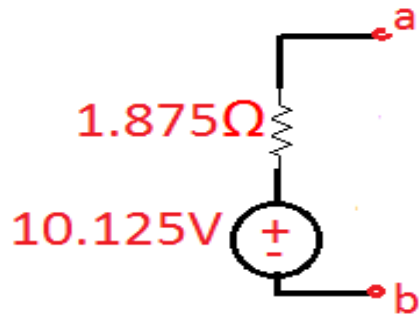

Step 3: To find  $i$  through  $10 \Omega$

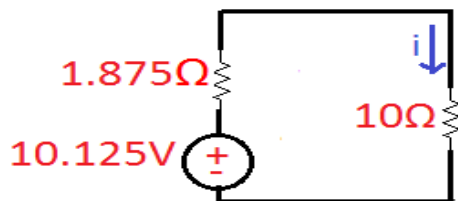Connect  $10 \Omega$  across terminals a-b




KVL:

$$-10.125 + 1.875i + 10i = 0$$


$$i = 0.85 \text{ A}$$

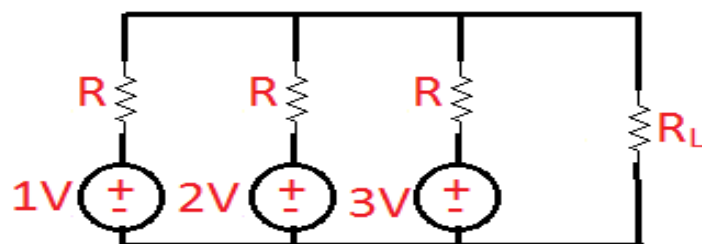P2. Find  $R$  such that the maximum Power delivered to the load is  $3\text{mW}$




Solution:

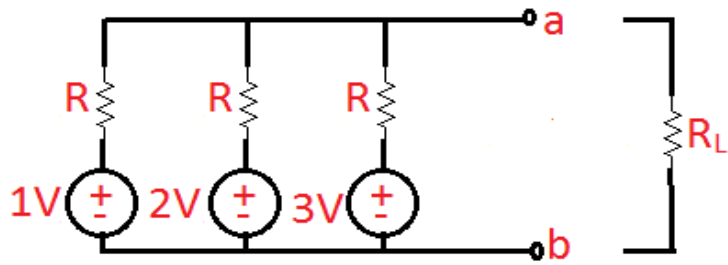Step 1: Remove  $R_L$  and mark the terminals a-b



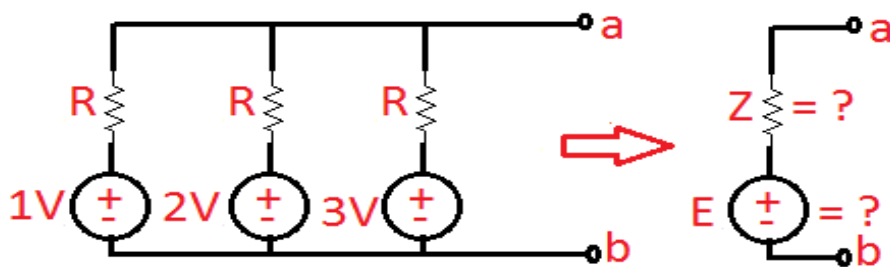Step 2: Using Millman's Theorem obtain one generator of emf E and internal impedance Z across a-b



To find E:

$$E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3}{Y_1 + Y_2 + Y_3}$$

$$E = \frac{1 \left(\frac{1}{R}\right) + 2 \left(\frac{1}{R}\right) + 3 \left(\frac{1}{R}\right)}{\frac{1}{R} + \frac{1}{R} + \frac{1}{R}}$$

$$E = \frac{6/R}{3/R} = 2V$$


$$E = 2V$$

To find Z:


$$Z = \frac{1}{Y_1 + Y_2 + Y_3}$$

$$Z = \frac{1}{\frac{1}{R} + \frac{1}{R} + \frac{1}{R}} = \frac{R}{3} \Omega$$


$$Z = \frac{R}{3} \Omega$$

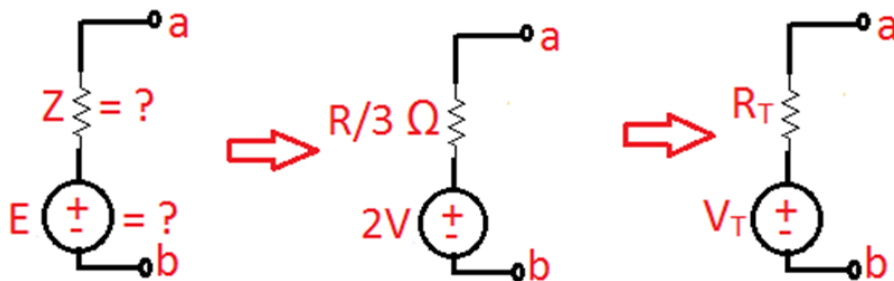

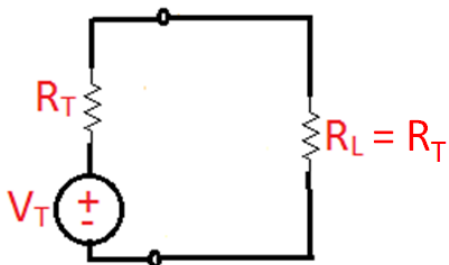Therefore by Maximum Power Transfer Theorem, for Maximum Power to be transferred to the load in DC circuits  $R_L = R_T$





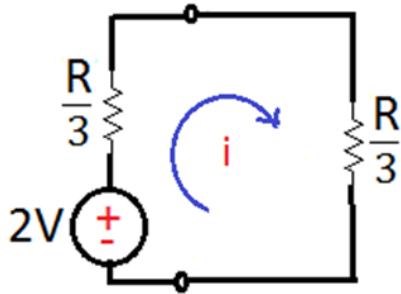

Applying KVL:

$$-2 + \frac{R}{3}i + \frac{R}{3}i = 0$$

$$i = \frac{3}{R}$$

To find R for  $P_{\max} = 3\text{mW}$

$$P_{\max} = i^2 R_L$$

$$3\text{m} = \left(\frac{3}{R}\right)^2 \frac{R}{3}$$

$$3\text{m} = \frac{9}{R^2} \frac{R}{3}$$

$$R = \frac{3}{3\text{m}} = 1\text{K}\Omega$$

Therefore  $1\text{K}\Omega$  Resistor has to be connected as the load resistor for maximum power of  $3\text{mW}$  to be delivered to the load.